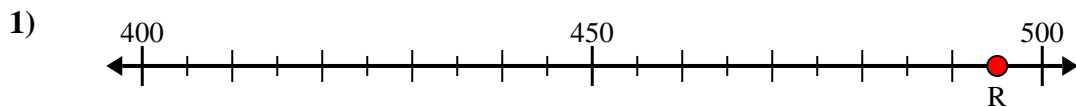





Find the value of R.


Answers




1. _____

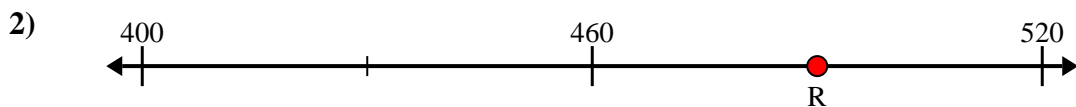


2. _____

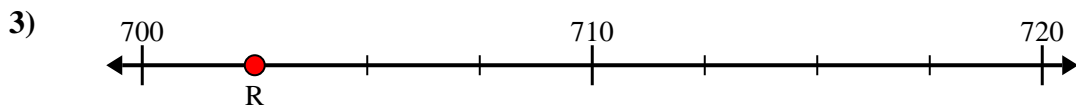


3. _____

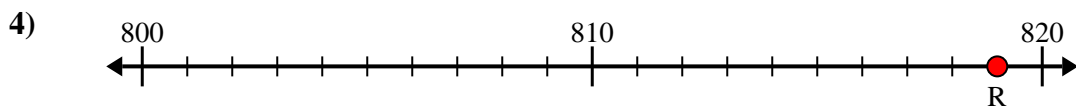


4. _____

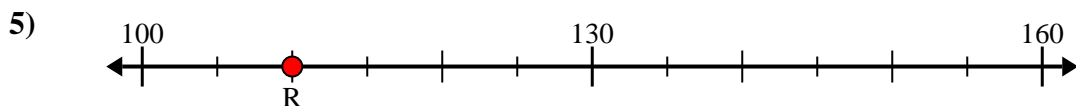


5. _____

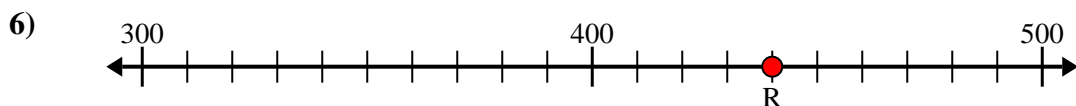


6. _____

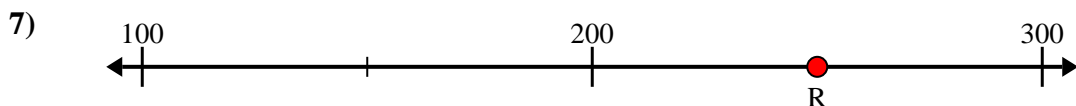


7. _____

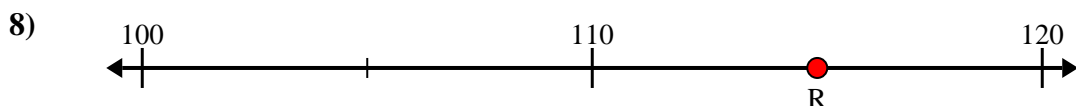

8. _____

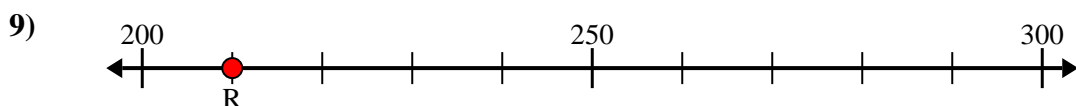











9. _____

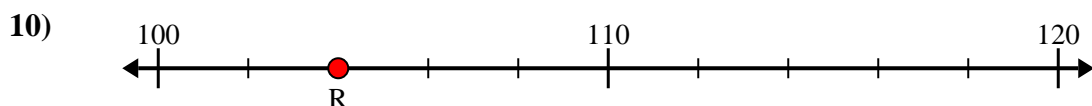

10. _____



Find the value of R.

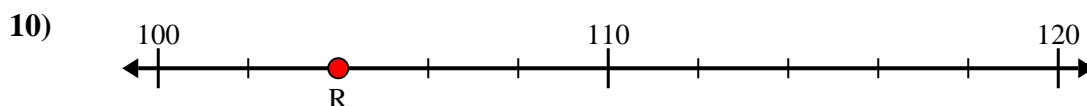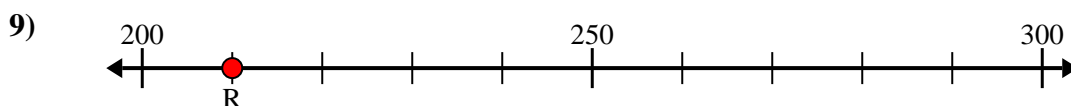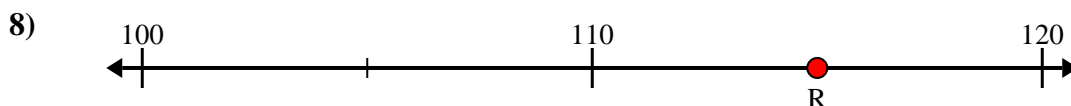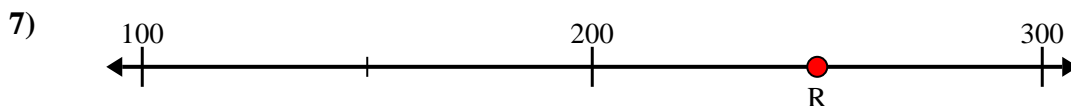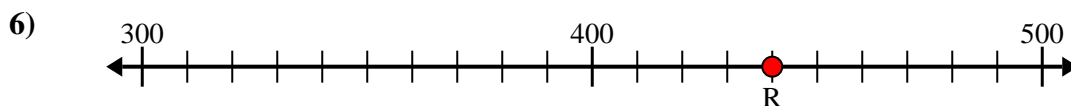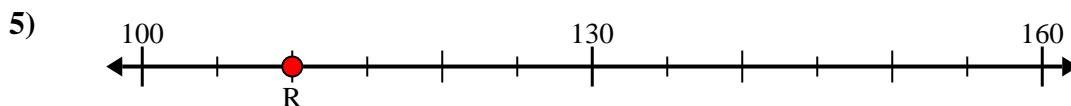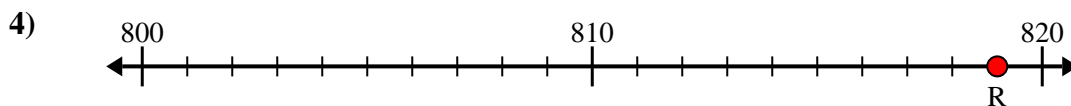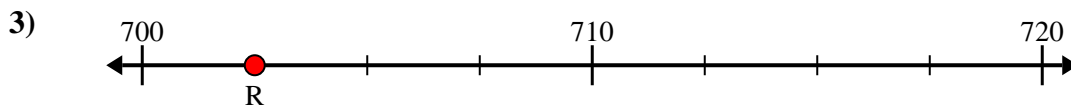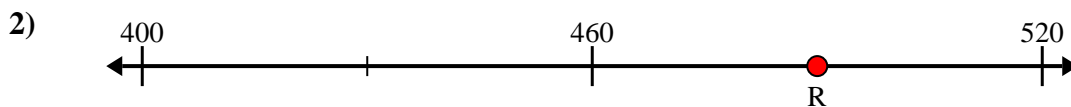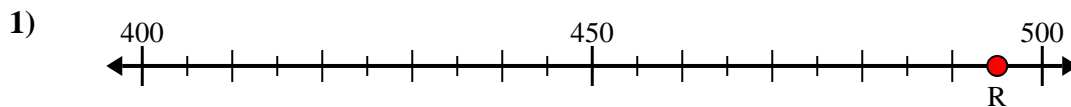Answers1. 4952. 4903. 702.54. 8195. 1106. 4407. 2508. 1159. 21010. 104