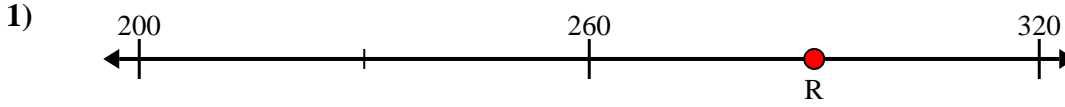





Find the value of R.


Answers



1. _____

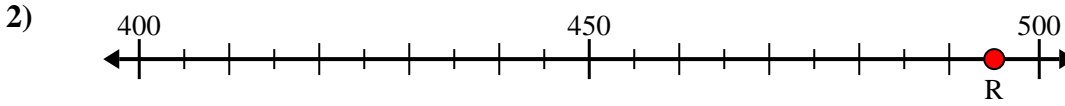


2. _____

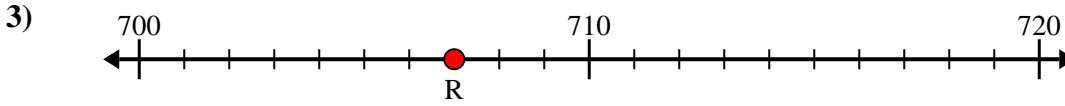


3. _____

4. _____

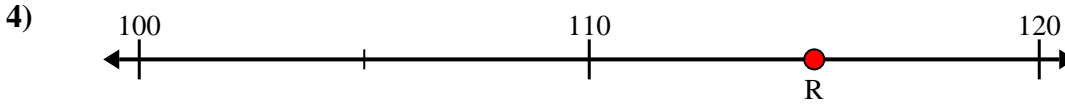


5. _____

6. _____

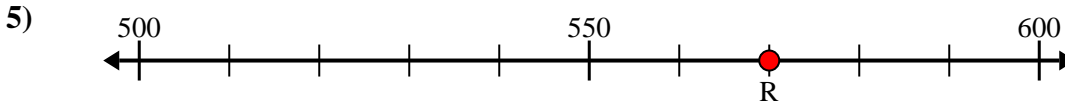




7. _____

8. _____

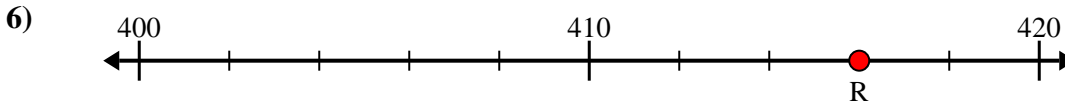











9. _____

10. _____

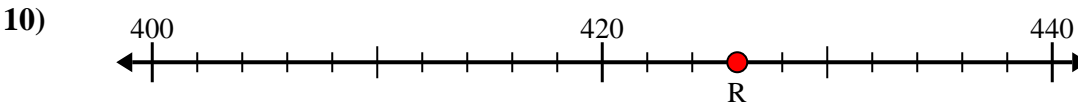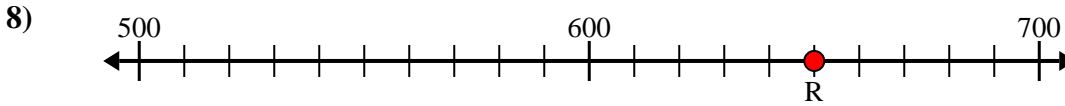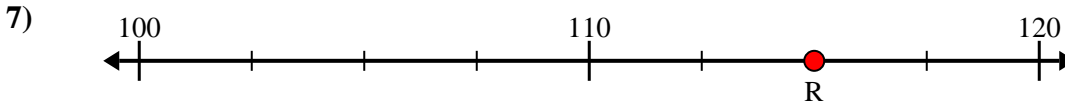



Find the value of R.

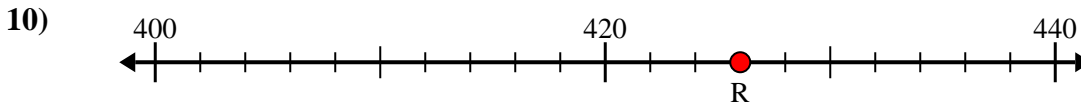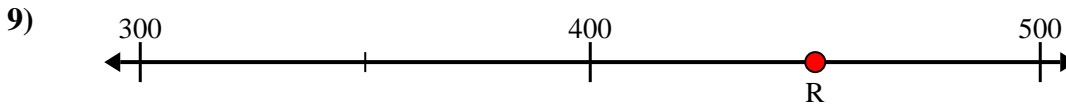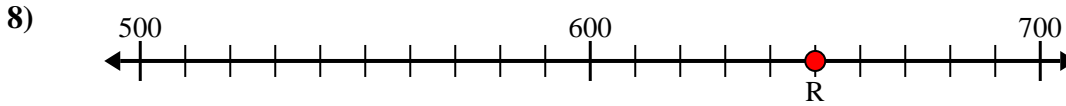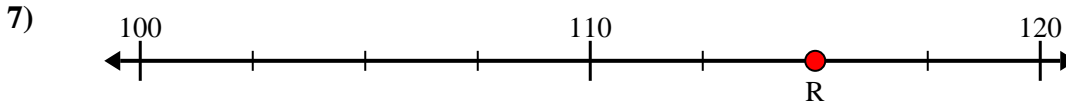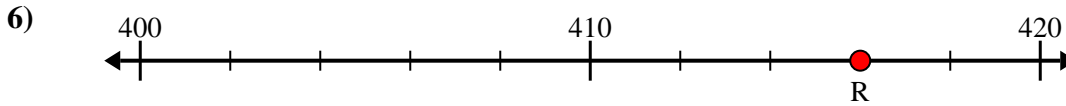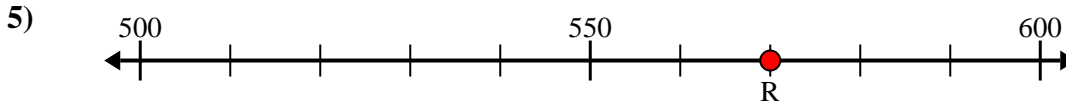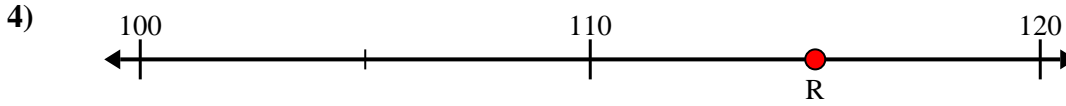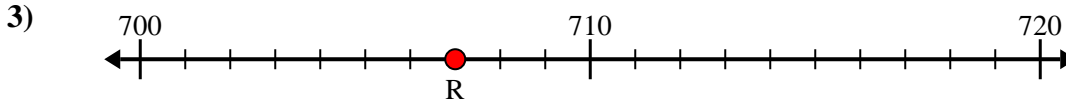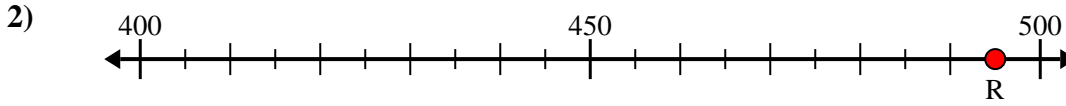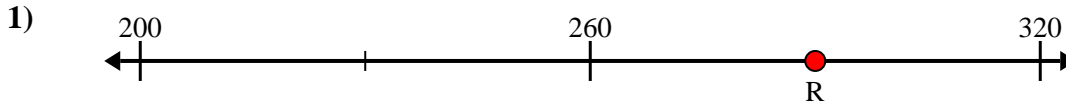

Answers

1. 290

2. 495

3. 707

4. 115

5. 570

6. 416

7. 115

8. 650

9. 450

10. 426